

Adder/Subtractor Circuit

By: Kyle W. Brown

Goals of the Experiment

To design an adder/subtractor circuit by combining lab 1 full adder circuit using MAX7008 family in Quartus 9. The full adder circuit has been created into a symbol to minimize the complexity of the circuit.

Theory of Operation

Adder/Subtractor circuit is combined into one circuit with one common binary adder. This is done by including an exclusive-OR gate with each full adder. The mode input M controls the operation. When M=0, the circuit is an adder, and when M=1, the circuit becomes a subtractor. The B inputs are all complemented and a 1 is added through the input carry. The circuit performs the operation A plus the 2's complement of B.

The range of binary numbers both signed and unsigned for the adder/subtractor circuit is 2^4 or 15_{10} and -16_{10} . An overflow occurs when two numbers of n digits each are added, and the sum occupies n+1 digits. The detection of an overflow after the addition of two binary numbers depends on whether the numbers are considered to be signed or unsigned. When two unsigned numbers are added an overflow is detected from the end carry out of the most significant position. The exclusive-OR is for detecting an overflow.

Use the following <u>data</u> (unsigned numbers) to show the proper operation of your circuit (the given numbers are in decimal): Addition	Subtraction
5 + 2	5 - 2
7 + 7	7 - 7
10 + 8	11 - 6
2 + 9	14 - 9
11 + 5	5 - 0
3 + 12	13 - 3




Truth Table

A_n	B_n	C_{n-1}	S_n	C_n
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Schematics of the Circuit

 The schematic below shows an 8x1 multiplexer with adder/subtractor connected by XOR gates to the black box or the full adder.



Experimental Results

Compilation Results


The schematic has been compiled below in order to expedite synthesis of the circuit. The results from the compilation were used as values for preparation of the waveform editor.

Flow Status	Successful - Mon Feb 12 12:42:42 2018
Quartus II Version	9.1 Build 350 03/24/2010 SP 2 SJ Web Edition
Revision Name	AdderSubtractor
Top-level Entity Name	AdderSubtractor
Family	MAX7000S
Device	EPM7128SLC84-7
Timing Models	Final
Met timing requirements	Yes
Total macrocells	11 / 128 (9 %)
Total pins	18 / 68 (26 %)

Flow: Compilation	
Task	Time
✓ Compile Design	00:00:14
✓ Analysis & Synthesis	00:00:07
✓ Fitter (Place & Route)	00:00:03
✓ Assembler (Generate programming files)	00:00:03
✓ Classic Timing Analysis	00:00:01
EDA Netlist Writer	
Program Device (Open Programmer)	

Simulation Results

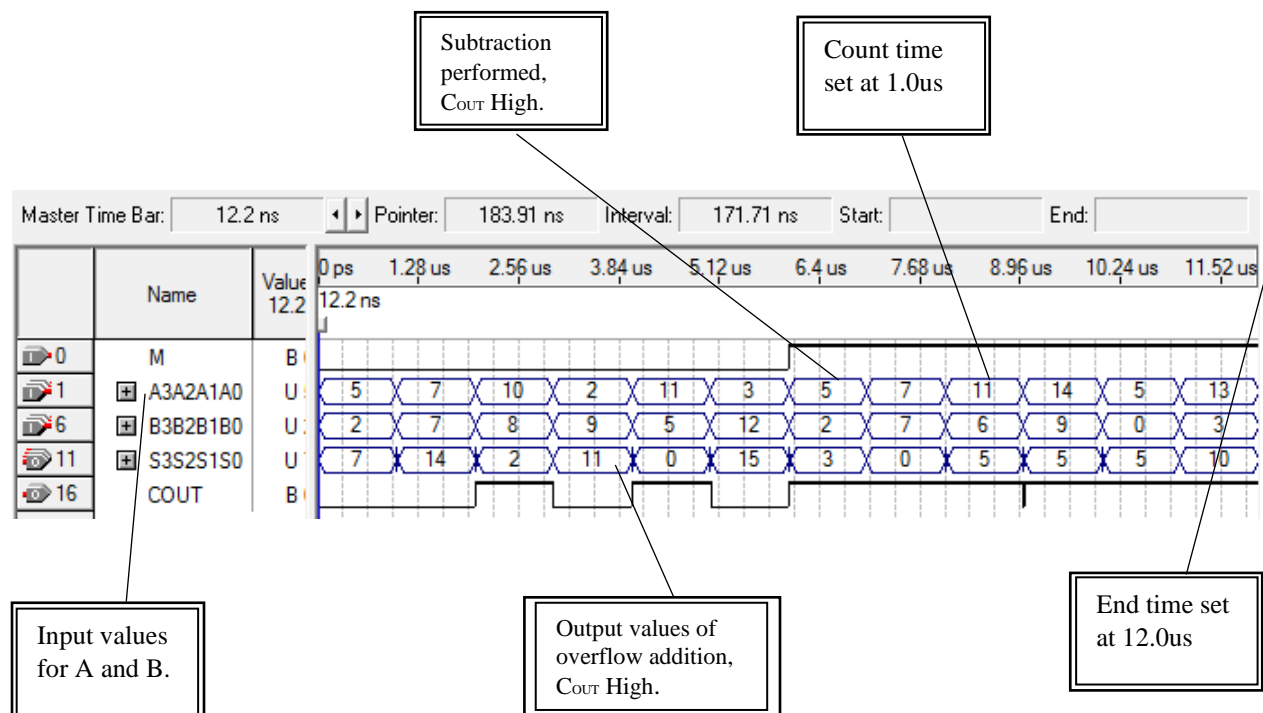Below is the Waveform for adder/subtractor circuit. The outputs for the addition and subtraction are correct. The simulation is based on a 12.0 us end time with a 1.0us count time.



Conclusion

The Truth table, schematic, compilation, and simulation for the adder/subtractor adder were successful. There were no errors to document in the compilation or simulation. The additions and subtractions were performed from the Theory of Operation table. The simulations success is documented below. The circuit will be suitable to proceed to lab 4.



Info: Number of transitions in simulation is 204

Info: Quartus II Simulator was successful. 0 errors, 0 warnings

